

Experiment - 9: Single and Dual Port RAM and ROM

Using Quartus Prime

NAME: Jayakrishnan Menon

REG NO: 22BEC1205

DATE: 12/03/2025

Aim:

Write a Verilog RTL code for Simulation and Implementation of Single and Dual Port RAM and ROM. Also, perform the simulation of the circuit using Quartus Prime and Model Sim. Finally, implement these circuits on the FPGA kit, "5CSXFC6D6F31C6N"

Software Required: Quartus Prime, ModelSim


Hardware Required: Altera Cyclone V 5CSXFC6D6F31C6N

Procedure:


- Open Quartus Prime 21.1.
- Go to File -> New Project wizard -> select Source folder & type file name -> Next.
- Select Empty Project in Project type -> Next.
- Click on Next in Add Files dialog box.
- Select "Cyclone V SX Extended Features" in Device Family.
- In available devices, select the one ending with "31C6" -> Next.
- Select the tool name as "ModelSim" and Format as "VerilogHDL" in simulation.
- Click on Finish. The project is now created.
- In the Task window, select RTL simulation and run, this would open the ModelSim window.
- Simulate the full adder as you would do using ModelSim by forcing the input values.
- In Compilation -> select compile design.
- Go to Assignments tab -> Pin planner -> Give the location for each i/o pin.
- Go to Hardware Setup -> Select USB.
- Change the file to Fulladder.v in the program/configure option and select Start.

Theory

- A single port memory is a type of memory that can be accessed by only one device or process at a time. In this type of memory, data can be written and read from the same port.
- It is generally used in applications where only one processor is used, and the memory is not required to be accessed by multiple processors simultaneously.
- A single-port RAM (Random Access Memory) is a type of digital memory component that allows data to be read from and written to a single memory location (address) at a time. It is a simple form of memory that provides a basic storage mechanism for digital systems.
- Each memory location in a single-port RAM can store a fixed number of bits (usually a power of 2, such as 8, 16, 32, etc.).

 

 - The recent technology has developed dual port memories. Now it is possible to access the same address locations through two ports.
- Dual port memories have simplified many problems in designing digital systems.
- Both ROM and RAM can be of dual port. The block diagram of a true dual port RAM is shown below.



Single Port RAM:


```
module singpram(
input [2:0] data,
input [5:0] addr,
input we, clk,
output [2:0] q
);
```

```
reg [2:0] ram[63:0];
reg [5:0] addr_reg;
```

```
always @(posedge clk)begin
// Write
if (we)
ram[addr] <= data;
addr_reg <= addr;
end
assign q = ram[addr_reg];
```

endmodule

Output:

 

Single Port ROM:


```
module singpram(  
    input [5:0] addr,  
    input clk,  
    output [3:0] q  
);  
reg [3:0] rom[63:0];  
reg [5:0] addr_reg;
```

```
initial begin  
    rom[0]=4'b0000;  
    rom[1]=4'b0001;  
    rom[2]=4'b0010;  
    rom[3]=4'b0011;  
    rom[4]=4'b0100;  
    rom[5]=4'b0101;  
    rom[6]=4'b0110;  
    rom[7]=4'b0111;  
    rom[8]=4'b1000;  
    rom[9]=4'b1001;  
    rom[10]=4'b1010;  
    rom[11]=4'b1011;  
    rom[12]=4'b1100;  
    rom[13]=4'b1101;  
    rom[14]=4'b1110;  
    rom[15]=4'b1111;  
end
```

```
always @ (posedge clk)begin  
    addr_reg <= addr;  
end
```

```
assign q = rom[addr_reg];  
endmodule
```


Output:

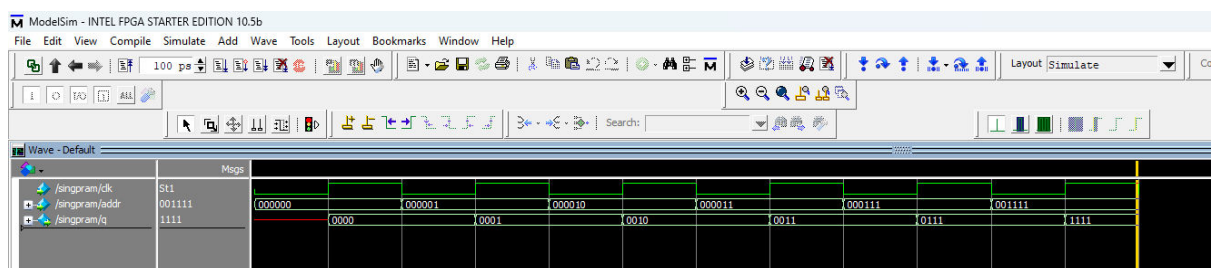

Dual Port RAM:

```
module Dual_Port_RAM (  
    input clk,  
    input we_a,  
    input we_b,  
    input [3:0] addr_a,  
    input [3:0] addr_b,  
    input [7:0] din_a,  
    input [7:0] din_b,  
    output reg [7:0] dout_a,  
    output reg [7:0] dout_b  
);  
  
    reg [7:0] ram [15:0];  
  
    always @(posedge clk) begin  
        // Port A operations  
        if (we_a)  
            ram[addr_a] <= din_a;  
        dout_a <= ram[addr_a]; // Ensure read after write is handled correctly  
  
        // Port B operations  
        if (we_b)  
            ram[addr_b] <= din_b;  
        dout_b <= ram[addr_b]; // Ensure read after write is handled correctly  
    end  
endmodule
```


Output:

 

Dual Port ROM:

```
module Dual_Port_ROM (  
    input [3:0] addr_a, addr_b, // Two 4-bit address inputs  
    output reg [7:0] data_a, data_b // Two 8-bit data outputs  
);  
  
// ROM Memory Initialization (Preloaded values)  
reg [7:0] rom [15:0];  
initial begin  
    rom[0] = 8'h12; rom[1] = 8'h34; rom[2] = 8'h56; rom[3] = 8'h78;  
    rom[4] = 8'h9A; rom[5] = 8'hBC; rom[6] = 8'hDE; rom[7] = 8'hF0;  
    rom[8] = 8'h11; rom[9] = 8'h22; rom[10] = 8'h33; rom[11] = 8'h44;  
    rom[12] = 8'h55; rom[13] = 8'h66; rom[14] = 8'h77; rom[15] = 8'h88;  
end  
  
always @(*) begin  
    data_a = rom[addr_a]; // Read data from address A  
    data_b = rom[addr_b]; // Read data from address B  
end  
  
endmodule
```

Output:

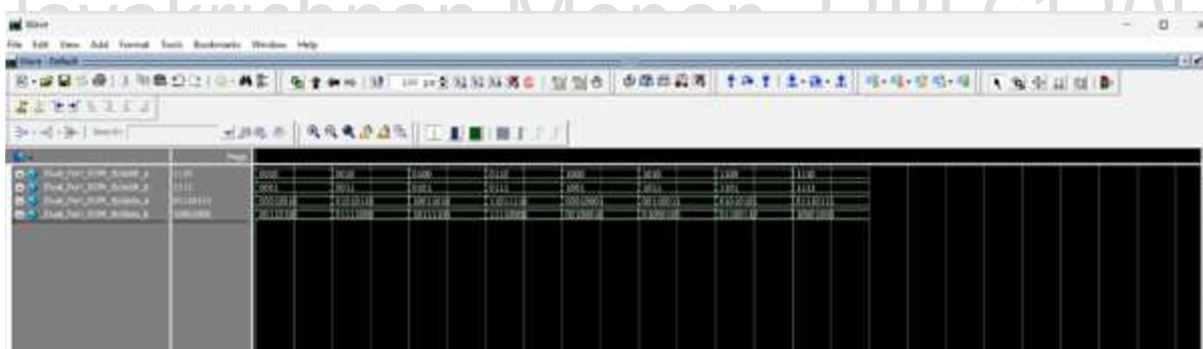

| addr_a | addr_b | data_a | data_b |
|--------|--------|--------|--------|
| 0000 | 0000 | 0000 | 0000 |
| 0000 | 0001 | 0000 | 0001 |
| 0000 | 0010 | 0000 | 0010 |
| 0000 | 0011 | 0000 | 0011 |
| 0000 | 0100 | 0000 | 0100 |
| 0000 | 0101 | 0000 | 0101 |
| 0000 | 0110 | 0000 | 0110 |
| 0000 | 0111 | 0000 | 0111 |
| 0000 | 1000 | 0000 | 1000 |
| 0000 | 1001 | 0000 | 1001 |
| 0000 | 1010 | 0000 | 1010 |
| 0000 | 1011 | 0000 | 1011 |
| 0000 | 1100 | 0000 | 1100 |
| 0000 | 1101 | 0000 | 1101 |
| 0000 | 1110 | 0000 | 1110 |
| 0000 | 1111 | 0000 | 1111 |

Pin Planning: RAM (Single Port):

The screenshot shows the Pin Planner interface for Cyclone V - 5C5KFC6D6F31C6. The top view displays the pin grid with various pins assigned. The left sidebar shows the 'Groups' list with 'Node Name' and 'Direction' columns. The bottom table lists the pin assignments for RAM (Single Port).

| Node Name | Direction | Location | I/O Bank | VREF Group | I/O Standard | Reserved | Current Strength | Slew Rate | Differential Pair | Other Settings |
|-----------|-----------|----------|----------|------------|-----------------|----------|------------------|-------------|-------------------|----------------|
| add[5] | Input | PH1_V25 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[4] | Input | PH1_V25 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[3] | Input | PH1_A30 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[2] | Input | PH1_A28 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[1] | Input | PH1_Y27 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[0] | Input | PH1_A30 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| clk | Input | PH1_A14 | 3B | B3B_NO | 2.5 V (default) | | 12mA (default) | | | |
| data[2] | Input | PH1_A30 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| data[1] | Input | PH1_A30 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| data[0] | Input | PH1_A28 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| q[2] | Output | PH1_A23 | 4A | B4A_NO | 2.5 V (default) | | 12mA (default) | 1 (default) | | |
| q[1] | Output | PH1_A23 | 4A | B4A_NO | 2.5 V (default) | | 12mA (default) | 1 (default) | | |
| q[0] | Output | PH1_A24 | 5A | B5A_NO | 2.5 V (default) | | 12mA (default) | 1 (default) | | |
| we | Input | PH1_A30 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |


ROM (Single Port):

The screenshot shows the Pin Planner interface for Cyclone V - 5C5KFC6D6F31C6. The top view displays the pin grid with various pins assigned. The left sidebar shows the 'Groups' list with 'Node Name' and 'Direction' columns. The bottom table lists the pin assignments for ROM (Single Port).

| Node Name | Direction | Location | I/O Bank | VREF Group | I/O Standard | Reserved | Current Strength | Slew Rate | Differential Pair | Other Settings |
|-----------|-----------|----------|----------|------------|-----------------|----------|------------------|-------------|-------------------|----------------|
| add[5] | Input | PH1_V25 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[4] | Input | PH1_V25 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[3] | Input | PH1_A30 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[2] | Input | PH1_A28 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[1] | Input | PH1_Y27 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| add[0] | Input | PH1_A30 | 5B | B5B_NO | 2.5 V (default) | | 12mA (default) | | | |
| clk | Input | PH1_A14 | 3B | B3B_NO | 2.5 V (default) | | 12mA (default) | | | |
| q[2] | Output | PH1_A23 | 4A | B4A_NO | 2.5 V (default) | | 12mA (default) | 1 (default) | | |
| q[1] | Output | PH1_A23 | 4A | B4A_NO | 2.5 V (default) | | 12mA (default) | 1 (default) | | |
| q[0] | Output | PH1_A24 | 5A | B5A_NO | 2.5 V (default) | | 12mA (default) | 1 (default) | | |


RTL Viewer:

RAM (Single Port):

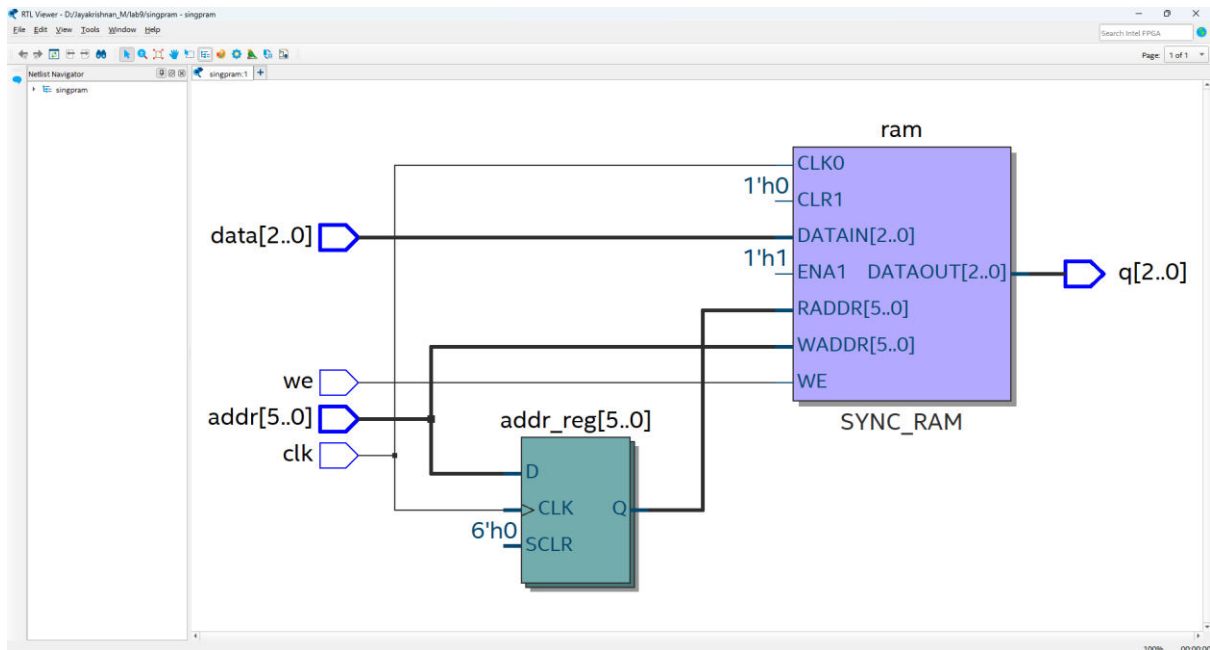


Jayakrishnan Menon 22BEC1205

ROM (Single Port):

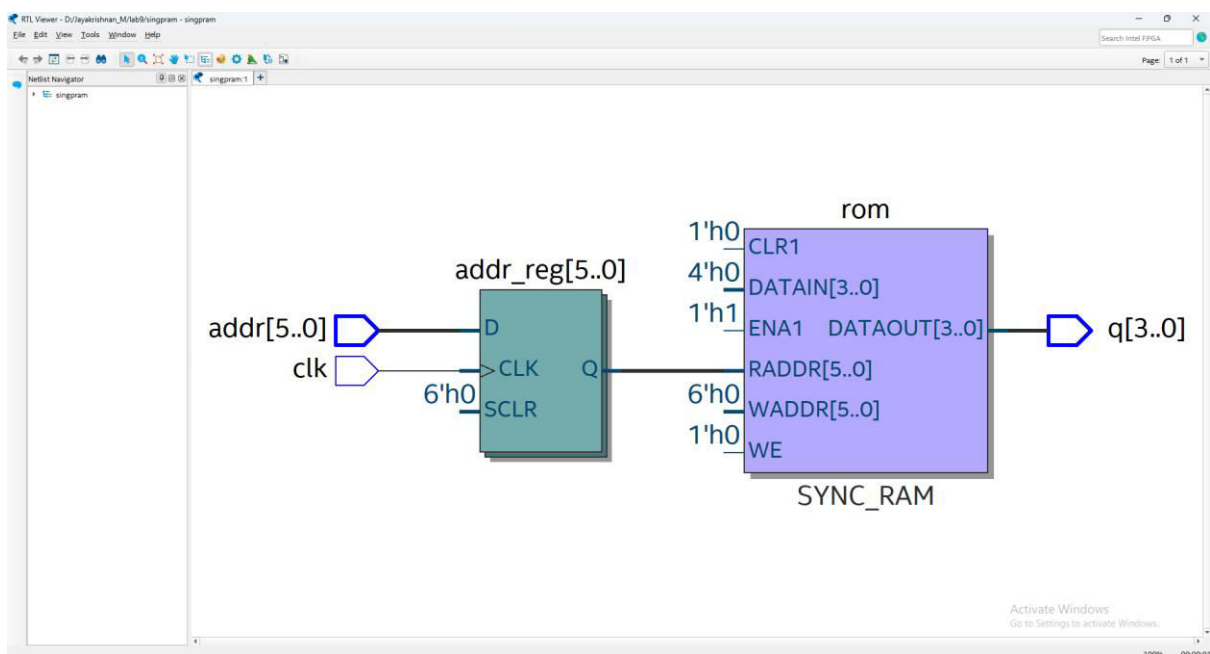


Technology Map Viewer:

RAM (Single Port):

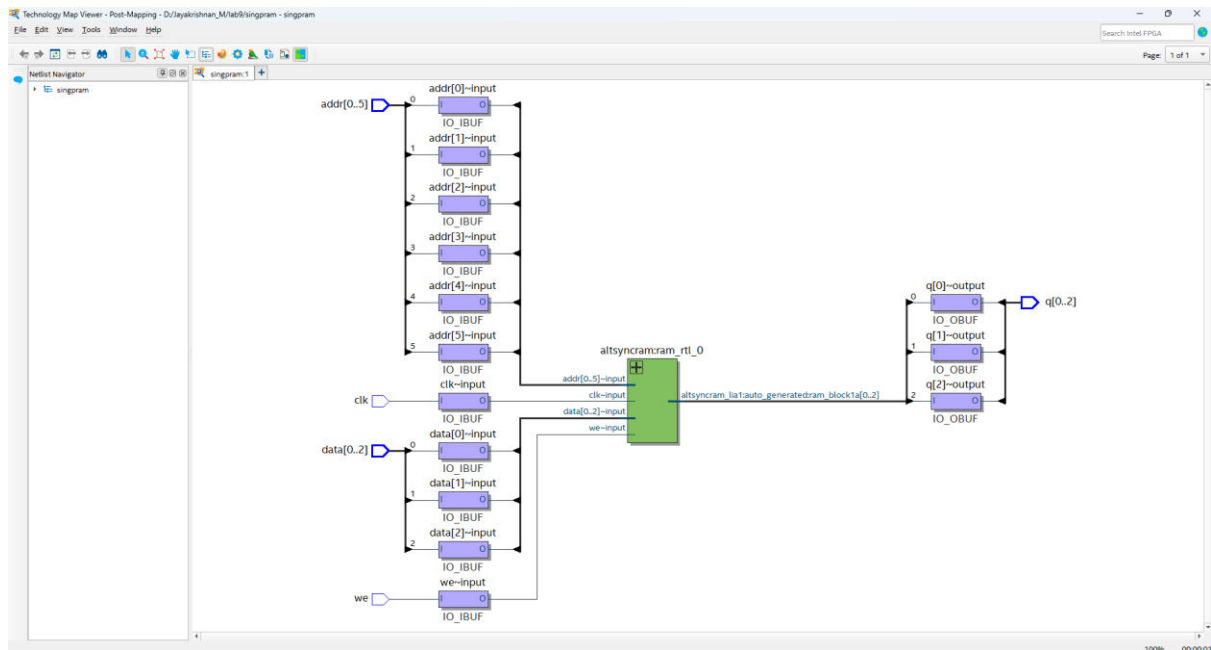

Jayakrishnan Menon 22BEC1205

ROM (Single Port):

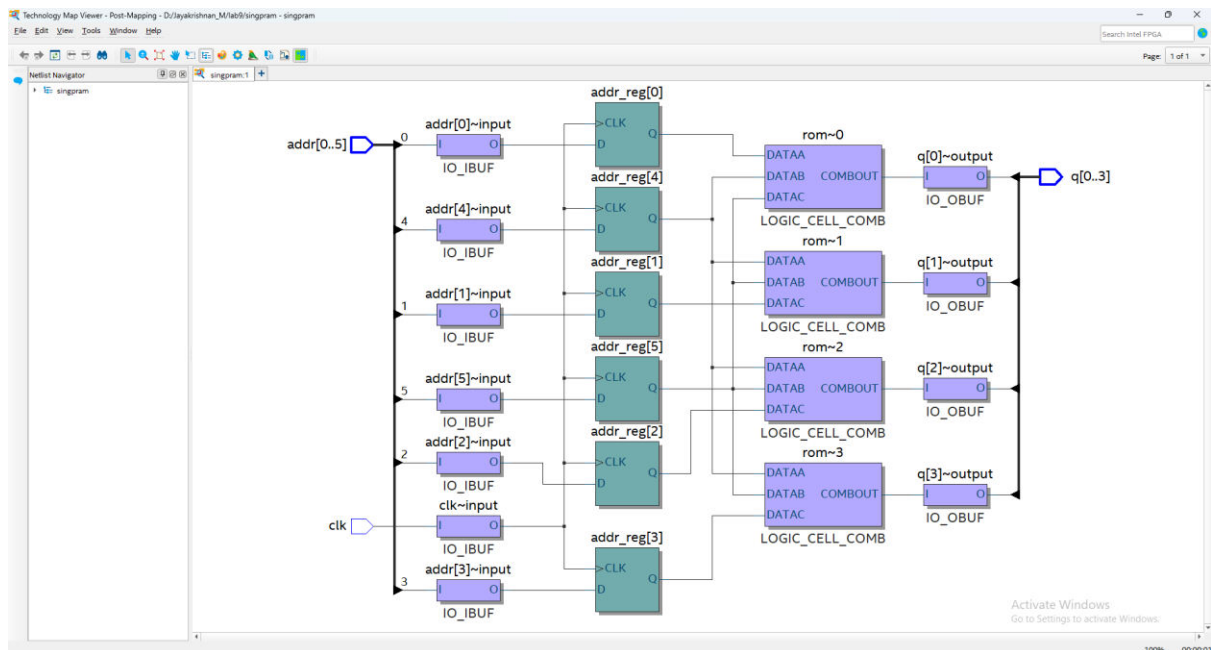

Logic Utilization:

RAM (Single Port):

| | | | |
|----------------------------------|--|---|--|
| singpram.v X | | Compilation Report - singpram X | |
| Table of Contents | | Flow Summary | |
| Flow Summary | | <<Filter>> | |
| Flow Settings | | Flow Status | |
| Flow Non-Default Global Settings | | Successful - Mon Mar 10 10:39:00 2025 | |
| Flow Elapsed Time | | Quartus Prime Version | |
| Flow OS Summary | | 21.1.0 Build 842 10/21/2021 SJ Lite Edition | |
| Flow Log | | Revision Name | |
| Analysis & Synthesis | | singpram | |
| Fitter | | Top-level Entity Name | |
| Assembler | | singpram | |
| Timing Analyzer | | Family | |
| EDA Netlist Writer | | Cyclone V | |
| Flow Messages | | Device | |
| Flow Suppressed Messages | | 5CSXFC6D6F31C6 | |
| | | Timing Models | |
| | | Final | |
| | | Logic utilization (in ALMs) | |
| | | 1 / 41,910 (< 1 %) | |
| | | Total registers | |
| | | 0 | |
| | | Total pins | |
| | | 14 / 499 (3 %) | |
| | | Total virtual pins | |
| | | 0 | |
| | | Total block memory bits | |
| | | 192 / 5,662,720 (< 1 %) | |
| | | Total DSP Blocks | |
| | | 0 / 112 (0 %) | |
| | | Total HSSI RX PCSs | |
| | | 0 / 9 (0 %) | |
| | | Total HSSI PMA RX Deserializers | |
| | | 0 / 9 (0 %) | |
| | | Total HSSI TX PCSs | |
| | | 0 / 9 (0 %) | |
| | | Total HSSI PMA TX Serializers | |
| | | 0 / 9 (0 %) | |
| | | Total PLLs | |
| | | 0 / 15 (0 %) | |
| | | Total DLLs | |
| | | 0 / 4 (0 %) | |

ROM (Single Port):

| | | | |
|----------------------------------|--|---|--|
| Table of Contents | | Flow Summary | |
| Flow Summary | | <<Filter>> | |
| Flow Settings | | Flow Status | |
| Flow Non-Default Global Settings | | Successful - Mon Mar 10 11:14:21 2025 | |
| Flow Elapsed Time | | Quartus Prime Version | |
| Flow OS Summary | | 21.1.0 Build 842 10/21/2021 SJ Lite Edition | |
| Flow Log | | Revision Name | |
| Analysis & Synthesis | | singpram | |
| Fitter | | Top-level Entity Name | |
| Assembler | | singpram | |
| Timing Analyzer | | Family | |
| EDA Netlist Writer | | Cyclone V | |
| Flow Messages | | Device | |
| Flow Suppressed Messages | | 5CSXFC6D6F31C6 | |
| | | Timing Models | |
| | | Final | |
| | | Logic utilization (in ALMs) | |
| | | 3 / 41,910 (< 1 %) | |
| | | Total registers | |
| | | 6 | |
| | | Total pins | |
| | | 11 / 499 (2 %) | |
| | | Total virtual pins | |
| | | 0 | |
| | | Total block memory bits | |
| | | 0 / 5,662,720 (0 %) | |
| | | Total DSP Blocks | |
| | | 0 / 112 (0 %) | |
| | | Total HSSI RX PCSs | |
| | | 0 / 9 (0 %) | |
| | | Total HSSI PMA RX Deserializers | |
| | | 0 / 9 (0 %) | |
| | | Total HSSI TX PCSs | |
| | | 0 / 9 (0 %) | |
| | | Total HSSI PMA TX Serializers | |
| | | 0 / 9 (0 %) | |
| | | Total PLLs | |
| | | 0 / 15 (0 %) | |
| | | Total DLLs | |
| | | 0 / 4 (0 %) | |

Timing Analysis:

RAM (Single Port):

| Table of Contents | | Flow Elapsed Time | | | | |
|--|----------------------|-------------------|-------------------------|---------------------|------------------------------------|--|
| <ul style="list-style-type: none">Flow SummaryFlow SettingsFlow Non-Default Global SettingsFlow Elapsed TimeFlow OS SummaryFlow LogAnalysis & SynthesisFitterAssemblerTiming AnalyzerEDA Netlist WriterFlow MessagesFlow Suppressed Messages | | <<Filter>> | | | | |
| | Module Name | Elapsed Time | Average Processors Used | Peak Virtual Memory | Total CPU Time (on all processors) | |
| 1 | Analysis & Synthesis | 00:00:07 | 1.0 | 4817 MB | 00:00:07 | |
| 2 | Fitter | 00:00:22 | 1.0 | 6765 MB | 00:00:34 | |
| 3 | Assembler | 00:00:05 | 1.0 | 4886 MB | 00:00:03 | |
| 4 | Timing Analyzer | 00:00:03 | 1.0 | 5184 MB | 00:00:02 | |
| 5 | EDA Netlist Writer | 00:00:00 | 1.0 | 4737 MB | 00:00:00 | |
| 6 | Total | 00:00:37 | -- | -- | 00:00:46 | |

ROM (Single Port):


| Table of Contents | | Flow Elapsed Time | | | | |
|--|----------------------|-------------------|-------------------------|---------------------|------------------------------------|--|
| <ul style="list-style-type: none">Flow SummaryFlow SettingsFlow Non-Default Global SettingsFlow Elapsed TimeFlow OS SummaryFlow LogAnalysis & SynthesisFitterAssemblerTiming AnalyzerEDA Netlist WriterFlow MessagesFlow Suppressed Messages | | <<Filter>> | | | | |
| | Module Name | Elapsed Time | Average Processors Used | Peak Virtual Memory | Total CPU Time (on all processors) | |
| 1 | Analysis & Synthesis | 00:00:05 | 1.0 | 4844 MB | 00:00:06 | |
| 2 | Fitter | 00:00:27 | 1.0 | 6746 MB | 00:00:40 | |
| 3 | Assembler | 00:00:04 | 1.0 | 4892 MB | 00:00:03 | |
| 4 | Timing Analyzer | 00:00:03 | 1.0 | 5150 MB | 00:00:02 | |
| 5 | EDA Netlist Writer | 00:00:00 | 1.0 | 4738 MB | 00:00:00 | |
| 6 | Total | 00:00:39 | -- | -- | 00:00:51 | |

Jayakrishnan Menon 22BEC1205


Hardware Implementation:

RAM (Single Port):

Location:000000 Data:111

 


Location:010101 Data:011

 


ROM (Single Port):

Location:000011 Data:0011

 

Location:001111 Data:1111

 

Result:

Hence, Verilog RTL codes were successfully verified and implemented using Quartus Prime. The given task was completed successfully

Jayakrishnan Menon 22BEC1205