

## **Experiment - 7: FSM Based Vending Machine Simulation** **Using Quartus Prime**

**NAME:** Jayakrishnan Menon

**REG NO:** 22BEC1205

**DATE:** 17/02/2025

### **Aim:**

Write a Verilog RTL code for Simulation and Implementation of n FSM based Vending Machine. Also, perform the simulation of the Full Adder using Quartus Prime and Model Sim. Finally, implement these circuits on the FPGA kit, "5CSXFC6D6F31C6N"

**Software Required:** Quartus Prime, ModelSim

**Hardware Required:** Altera Cyclone V 5CSXFC6D6F31C6N

### **Procedure:**

- Open Quartus Prime 21.1.
- Go to File -> New Project wizard -> select Source folder & type file name -> Next.
- Select Empty Project in Project type -> Next.
- Click on Next in Add Files dialog box.
- Select "Cyclone V SX Extended Features" in Device Family.
- In available devices, select the one ending with "31C6" -> Next.
- Select the tool name as "ModelSim" and Format as "VerilogHDL" in simulation.
- Click on Finish. The project is now created.
- In the Task window, select RTL simulation and run, this would open the ModelSim window.
- Simulate the full adder as you would do using ModelSim by forcing the input values.
- In Compilation -> select compile design.
- Go to Assignments tab -> Pin planner -> Give the location for each i/o pin.
- Go to Hardware Setup -> Select USB.
- Change the file to Fulladder.v in the program/configure option and select Start.

## **Theory**

The operation of an FSM based vending machine can be described using a mathematical model with a finite number of states, where the machine transitions between these states based on input signals like coin insertions or button presses, ultimately dispensing a product when the correct amount is received and a selection is made; essentially, it's a way to represent the vending machine's behaviour as a series of logical steps with clear defined states like "idle," "accepting coins," "selecting product," and "dispensing item."

### **Key points about vending machine FSMs:**

States:

Each state represents a specific point in the vending machine's operation, like "waiting for input," "collecting coins," "calculating total amount," "ready to dispense".

Transitions:

Movements between states are triggered by input signals like coin insertion, button presses, or sensors detecting the presence of a product.

Inputs:

These are the signals that cause the machine to change states, usually including coin values or product selection buttons.

Outputs:

Actions taken based on the current state, such as displaying the current amount collected or activating the dispensing mechanism.

### **Benefits of using FSM for vending machines:**

Clear design process:

Helps visualize the complex logic of a vending machine by breaking it down into simple states and transitions.

Easy implementation:

Can be readily implemented in hardware using logic circuits or software to control the machine's behaviour.

Error detection:


By analysing state transitions, potential issues with the machine's logic can be identified.

### Lab Task:


To create a vending machine that dispenses a single product when the amount of money inserted reaches no more and no less than the set threshold.

To create a vending machine that dispenses multiple products, depending on the amount of money inserted.

FSM for 1<sup>st</sup> Task:

 

FSM for 2<sup>nd</sup> Task:

 

## Source code and Outputs:

### FSM for 1st Task:

```
module vendmach(input clk, rst, input [1:0]ip, output reg op);
```

```
reg [1:0]y,Y,A,B,C,D;
```

```
initial begin
```

```
A=2'b00; B=2'b01; C=2'b10; D=2'b11;
```

```
y=A; Y=2'bxx; op=1'b0;
```

```
//y=currentstate Y=nextstate op=currentoutput HEX1=op HEX0=st
```

```
end
```

```
always@(y,ip)begin //COMBINATIONAL LOGIC
```

```
case(y)
```

```
A: if(ip==2'b01)      begin Y=B; op=1'b0; end
```

```
    else if (ip==2'b10) begin Y=C; op=1'b0; end
```

```
    else if (ip==2'b00) begin Y=A; op=1'b0; end
```

```
B: if(ip==2'b01)      begin Y=C; op=1'b0; end
```

```
    else if (ip==2'b10) begin Y=D; op=1'b1; end
```

```
    else if (ip==2'b00) begin Y=B; op=1'b0; end
```

```
C: if(ip==2'b01)      begin Y=D; op=1'b1; end
```

```
    else if (ip==2'b10) begin Y=C; op=1'b0; end
```

```
    else if (ip==2'b00) begin Y=C; op=1'b0; end
```

```
D: if(ip==2'b01)      begin Y=B; op=1'b0; end
```

```
    else if (ip==2'b10) begin Y=C; op=1'b0; end
```

```
    else if (ip==2'b00) begin Y=D; op=1'b0; end
```

```
    else if (ip==2'b11) begin Y=A; op=1'b0; end //jump to start after transaction
```

```
default:  begin Y=2'bxx; op=1'bx; end
```

```
endcase
```

```
end
```

```
always@(posedge clk)begin //SEQUENTIAL PART
```


```
if(rst==1) begin y<=A;      end
```

```
else      begin y<=Y;      end
```

```
end
```

```
endmodule
```

## Output:

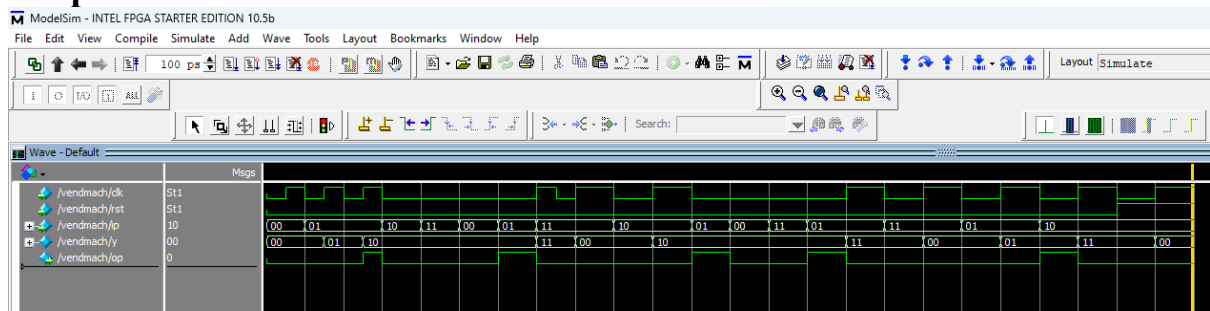

## FSM for 2nd Task:

```
module venmachm(
```

```
    input clk,
```

```
    input rst,
```

```
    input [1:0] coin,
```

```
    output reg chocolate,
```

```
    output reg chips,
```

```
    output reg biscuit
```

```
);
```

```
parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011, S4 = 3'b100;
```

```
reg[2:0] state,next_state;
```

```
always @(posedge clk or posedge rst) begin
```

```
    if (rst)
```

```
        state <= S0;
```

```
    else
```

```
        state <= next_state;
```

```
end
```

```
always @(*) begin
```

```
    next_state = state;
```

```
    chocolate = 0;
```

```
    chips=0;
```

```
    biscuit=0;
```

```
    case (state)
```

```
        S0: begin
```

```
            if (coin == 2'b01)
```

```
                next_state = S1;
```

```
            else if (coin == 2'b10)
```

```
                next_state = S2;
```

```
        end
```

```
        S1: begin
```

```

        if (coin == 2'b01)
            next_state = S2;
        else if (coin == 2'b10)
            next_state = S3;
        end
    S2: begin
biscuit =1;
        if (coin == 2'b01)
            next_state = S3;
        else if (coin == 2'b10)
            next_state = S4;
        end
    S3: begin
chocolate =1;
        if (coin == 2'b01)
            next_state = S4;
        end
    end
S4: begin
chips =1;
next_state = S0;
        end
    endcase
end

```


```

endmodule

module vending_machine_tb;
    reg clk;
    reg rst;
    reg [1:0] coin;
    wire chocolate, chips, biscuit;

```

**Output:**

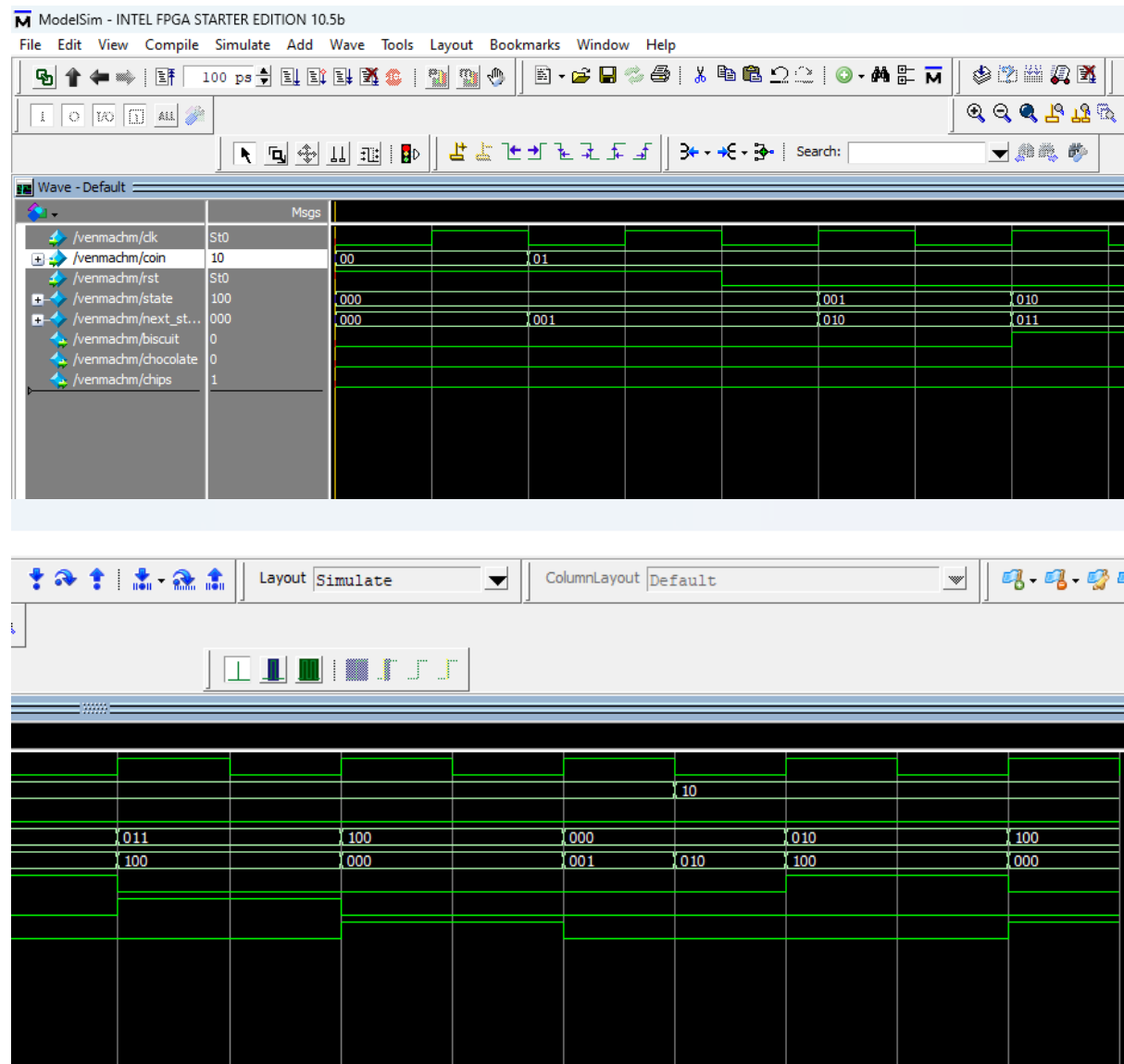

## Pin Planning:

For 1st Task:

Top View - Wire Bond  
Cyclone V - 5C5XFC6D6F31C6

Pin Legend:

- User I/O
- User assigned I/O
- Filter assigned I/O
- Unbonded pad
- Reserved pin
- DEV\_OE
- DFF\_n
- DFF\_p
- DFF\_n output
- DFF\_p output
- DO
- DQS
- DQS8
- Hard processor...
- CLK\_n
- CLK\_p
- GL\_n
- GL\_p
- Other PLL
- MSEL0
- MSEL1
- MSEL2
- MSEL3
- CONF\_DONE
- DCCLK
- nCE
- nCONFIG
- TDI
- TCK
- TMS
- TDO

Node Name	Direction	Location	I/O Bank	VREF Group	I/O Standard	Reserved	Current Strength	Slew Rate	Differential Pair	Other Analog Settings: GXB/VCC_T, GXB Vref, I/O Pin Term, indicated Refclk Ph, Common Mode Dr, triitter Slew Rate C, r Differential Outp, after Common Mo St
clk	Input	PN_194	3B	B3B_NO	2.5 V (default)		12mA (default)			
ip[1]	Input	PN_227	5B	B5B_NO	2.5 V (default)		12mA (default)			
ip[0]	Input	PN_230	5B	B5B_NO	2.5 V (default)		12mA (default)			
op	Output	PN_A024	5A	B5A_NO	2.5 V (default)		12mA (default)	1 (default)		
rst	Input	PN_A028	5B	B5B_NO	2.5 V (default)		12mA (default)			

For 2nd Task:

Top View - Wire Bond  
Cyclone V - 5C5XFC6D6F31C6

Pin Legend:


- User I/O
- User assigned I/O
- Filter assigned I/O
- Unbonded pad
- Reserved pin
- DEV\_OE
- DFF\_n
- DFF\_p
- DFF\_n output
- DFF\_p output
- DO
- DQS
- DQS8
- Hard processor...
- CLK\_n
- CLK\_p
- GL\_n
- GL\_p
- Other PLL
- MSEL0
- MSEL1
- MSEL2
- MSEL3
- CONF\_DONE
- DCCLK
- nCE
- nCONFIG
- TDI
- TCK

Node Name	Direction	Location	I/O Bank	VREF Group	I/O Standard	Reserved	Current Strength	Slew Rate	Differential Pair	Other Analog Settings: GXB/VCC_T, GXB Vref, I/O Pin Term, indicated Refclk Ph, Common Mode Dr, triitter Slew Rate C, r Differential Outp, after Common Mo St
brkout	Output	PN_A024	5A	B5A_NO	2.5 V (default)		12mA (default)	1 (default)		
choclate	Output	PN_A023	5A	B5A_NO	2.5 V (default)		12mA (default)	1 (default)		
clk	Input	PN_194	3B	B3B_NO	2.5 V (default)		12mA (default)			
com[1]	Input	PN_227	5B	B5B_NO	2.5 V (default)		12mA (default)			
com[0]	Input	PN_230	5B	B5B_NO	2.5 V (default)		12mA (default)			
rst	Input	PN_A028	5B	B5B_NO	2.5 V (default)		12mA (default)			




## RTL Viewer:

For 1st Task:

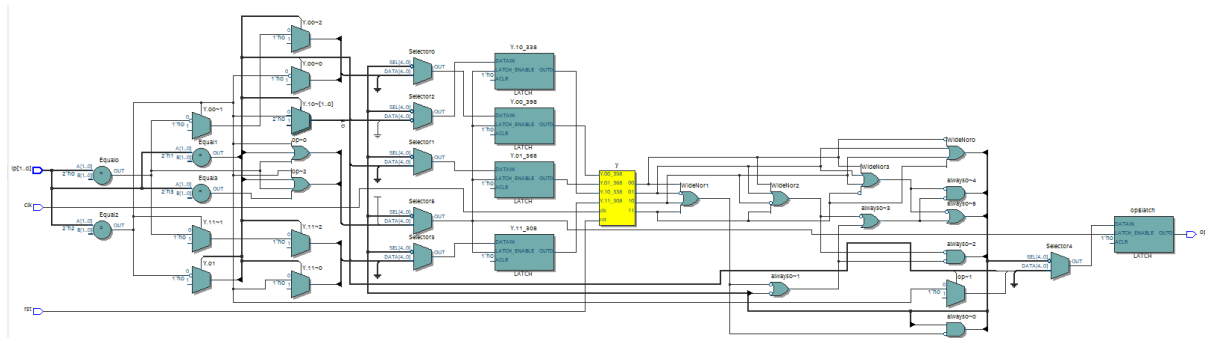


For 2nd Task:

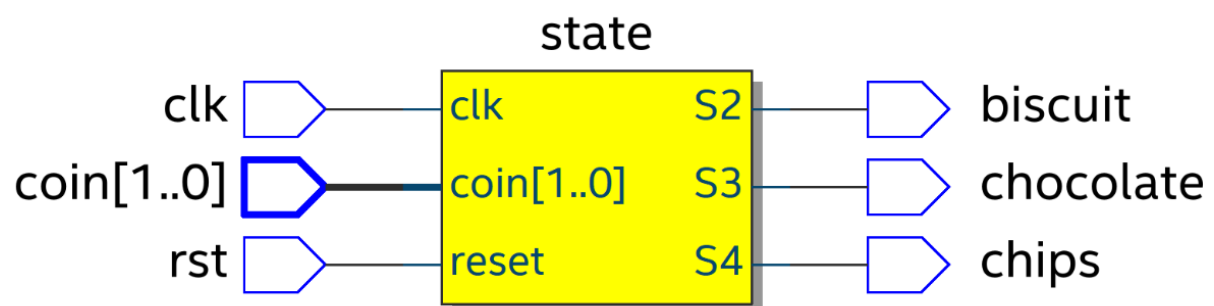


## Technology Map Viewer:


For 1st Task:

 


For 2nd Task:

 

For 1st Task:

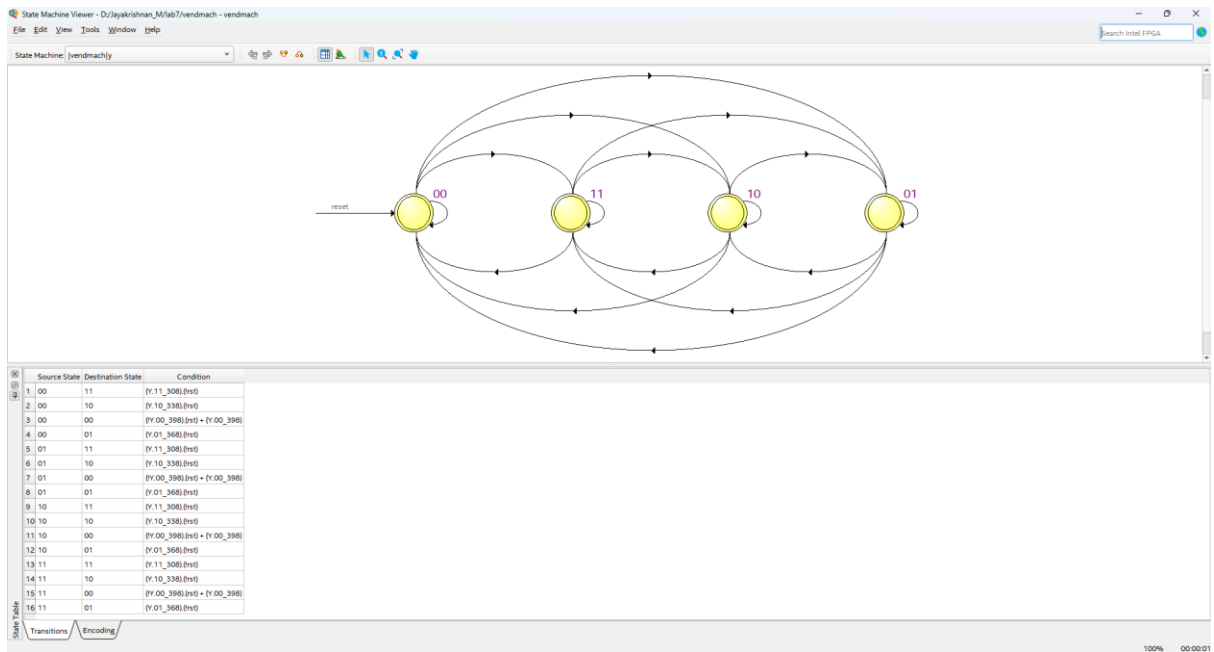


For 2nd Task:

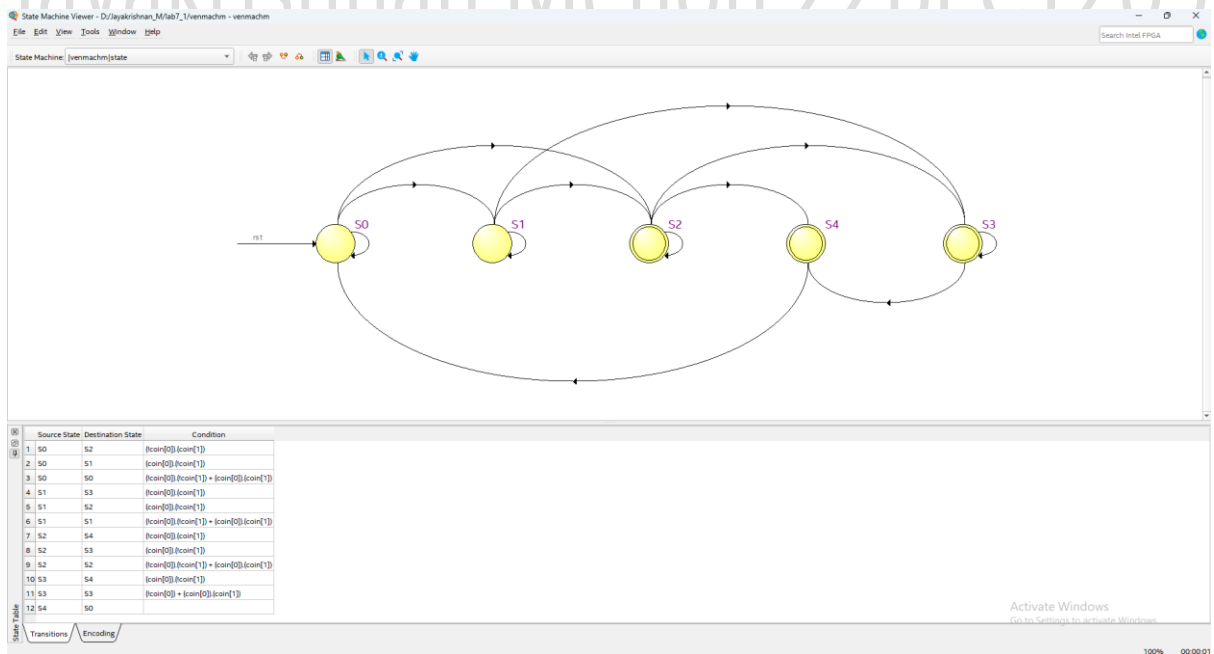


## Hardware Implementation:

For 1st Task:

State: S2, Input: 01, Output:1

 


State: S1, Input: 10, Output:1

 




For 2nd Task:


State: S2, Input: 01, Output: 1

 

State: S3, Input: 01, Output: 1

 

State: S4, Input: 01, Output: 1

 

Jayakrishnan Menon 22BEC1205

**Result:**

Hence, Verilog RTL codes for both Vending Machines were successfully verified and implemented using Quartus Prime. The given task was completed successfully