

Experiment - 5: Implementation of a 7-Segment Display to Show the Registration Number by Using Quartus Prime

NAME: Jayakrishnan Menon

REG NO: 22BEC1205

DATE: 06/01/2025

Aim:

Write a Verilog RTL code for designing and implementing a 7-segment Display. Also, perform the simulation of the Full Adder using Quartus Prime and ModelSim. Finally, implement the circuit on the FPGA kit, "5CSXFC6D6F31C6N"

Software Required: Quartus Prime, ModelSim


Hardware Required: Altera Cyclone V 5CSXFC6D6F31C6N

Procedure:

- Open Quartus Prime 21.1.
- Go to File -> New Project wizard -> select Source folder & type file name -> Next.
- Select Empty Project in Project type -> Next.
- Click on Next in Add Files dialog box.
- Select "Cyclone V SX Extended Features" in Device Family.
- In available devices, select the one ending with "31C6" -> Next.
- Select the tool name as "ModelSim" and Format as "VerilogHDL" in simulation.
- Click on Finish. The project is now created.
- In the Task window, select RTL simulation and run, this would open the ModelSim window.
- Simulate the full adder as you would do using ModelSim by forcing the input values.
- In Compilation -> select compile design.
- Go to Assignments tab -> Pin planner -> Give the location for each i/o pin.
- Go to Hardware Setup -> Select USB.
- Change the file to Fulladder.v in the program/configure option and select Start.

Theory

Seven segment displays are the output display device that provides a way to display information in the form of images or text or decimal numbers which is an alternative to the more complex dot matrix displays. It is widely used in digital clocks, basic calculators, electronic meters, and other electronic devices that display numerical information. It consists of seven segments of light-emitting diodes (LEDs) which are assembled like numerical 8.

 

Truth Table for an active high 7 segment display

(Note: in Cyclone V 5CSXFC6D6F31C6N the display logic is active low):

Inputs				Segments							
A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	For display 0
0	0	0	1	0	1	1	0	0	0	0	For display 1
0	0	1	0	1	1	0	1	1	0	1	For display 2
0	0	1	1	1	1	1	1	0	0	1	For display 3
0	1	0	0	0	1	1	0	0	1	1	For display 4
0	1	0	1	1	0	1	1	0	1	1	For display 5
0	1	1	0	1	0	1	1	1	1	1	For display 6
0	1	1	1	1	1	1	0	0	0	0	For display 7
1	0	0	0	1	1	1	1	1	1	1	For display 8
1	0	0	1	1	1	1	1	0	1	1	For display 9
1	0	1	0	1	1	1	0	1	1	1	For display A
1	0	1	1	0	0	1	1	1	1	1	For display b
1	1	0	0	1	0	0	1	1	1	0	For display C
1	1	0	1	0	1	1	1	1	0	1	For display d
1	1	1	0	1	0	0	1	1	1	1	For display E
1	1	1	1	1	0	0	0	1	1	1	For display F

Source code and Outputs:

```
module sevseg(
    input wire clk,
    output reg [6:0] HEX0,
    output reg [6:0] HEX1,
    output reg [6:0] HEX2,
    output reg [6:0] HEX3,
    output reg [6:0] HEX4,
    output reg [6:0] HEX5
);
integer i=0,j=0;
// 7-segment encoding (Common Anode: Active LOW)
function [6:0] seg_decode;
    input [3:0] digit;
    case (digit)
        4'h0: seg_decode = 7'b1000000;
        4'h1: seg_decode = 7'b1111001;
        4'h2: seg_decode = 7'b0100100;
        4'h3: seg_decode = 7'b0110000;
        4'h4: seg_decode = 7'b0011001;
        4'h5: seg_decode = 7'b0010010;
        4'h6: seg_decode = 7'b0000010;
        4'h7: seg_decode = 7'b1111000;
        4'h8: seg_decode = 7'b0000000;
        4'h9: seg_decode = 7'b0010000;
        4'hE: seg_decode = 7'b0000110;
        4'hC: seg_decode = 7'b1000110;
        default: seg_decode = 7'b1111111;
    endcase
endfunction


always@(posedge clk) begin
    if(i==0)begin
        HEX0 = seg_decode(4'h7);
        HEX1 = seg_decode(4'h8);
        HEX2 = seg_decode(4'h0);
        HEX3 = seg_decode(4'h1);
        HEX4 = seg_decode(4'hC);
        HEX5 = seg_decode(4'hE);
    end
    if(i==1)begin
        HEX0 = seg_decode(4'h5);
        HEX1 = seg_decode(4'h0);
        HEX2 = seg_decode(4'h2);
        HEX3 = seg_decode(4'h1);
        HEX4 = seg_decode(4'hC);
        HEX5 = seg_decode(4'hE);
    end
    j=j+1;
end
```

```
i=j%2;
```


```
end
```

```
endmodule
```


Output:

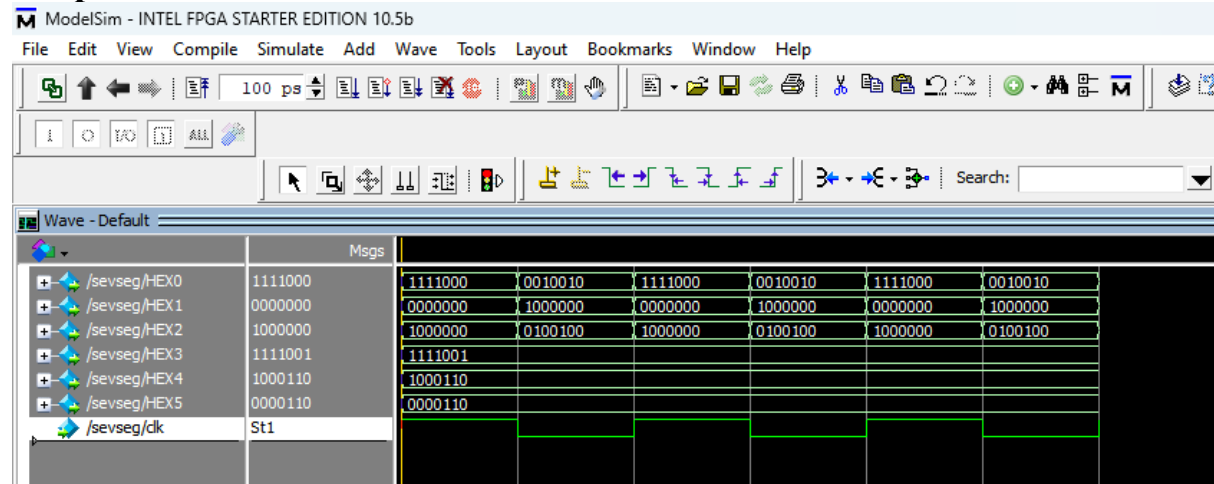


RTL Viewer:

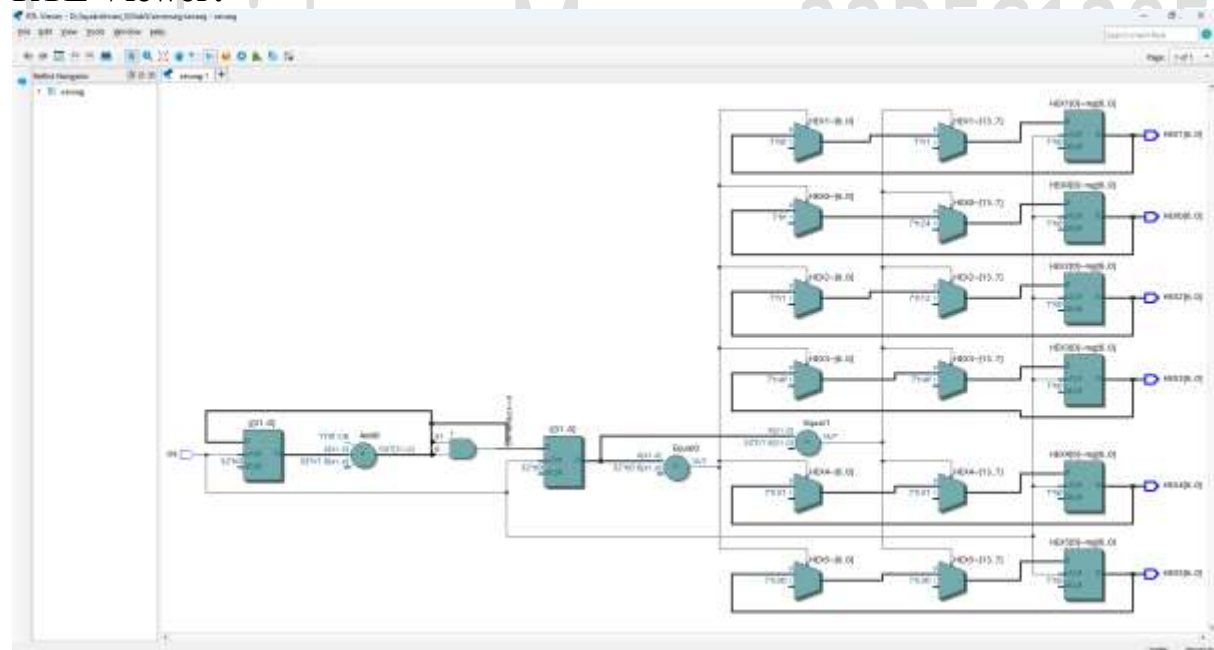

Technology Map Viewer:

 

Pin Planning:

 


Choosing on board 7 Segment Displays:

Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location	I/O Standard	Reserved	Current Strength	Slew Rate
HEX0[6]	Output	PM_AH18	4A	B4A_NO	PM_AH18	2.5 V		12mA (default)	1 (default)
HEX0[5]	Output	PM_AG18	4A	B4A_NO	PM_AG18	2.5 V		12mA (default)	1 (default)
HEX0[4]	Output	PM_AH17	4A	B4A_NO	PM_AH17	2.5 V		12mA (default)	1 (default)
HEX0[3]	Output	PM_AG16	4A	B4A_NO	PM_AG16	2.5 V		12mA (default)	1 (default)
HEX0[2]	Output	PM_AG17	4A	B4A_NO	PM_AG17	2.5 V		12mA (default)	1 (default)
HEX0[1]	Output	PM_V18	4A	B4A_NO	PM_V18	2.5 V		12mA (default)	1 (default)
HEX0[0]	Output	PM_W17	4A	B4A_NO	PM_W17	2.5 V		12mA (default)	1 (default)
HEX1[6]	Output	PM_V17	4A	B4A_NO	PM_V17	2.5 V		12mA (default)	1 (default)
HEX1[5]	Output	PM_AE17	4A	B4A_NO	PM_AE17	2.5 V		12mA (default)	1 (default)
HEX1[4]	Output	PM_AE18	4A	B4A_NO	PM_AE18	2.5 V		12mA (default)	1 (default)
HEX1[3]	Output	PM_AD17	4A	B4A_NO	PM_AD17	2.5 V		12mA (default)	1 (default)
HEX1[2]	Output	PM_AE16	4A	B4A_NO	PM_AE16	2.5 V		12mA (default)	1 (default)
HEX1[1]	Output	PM_V16	4A	B4A_NO	PM_V16	2.5 V		12mA (default)	1 (default)
HEX1[0]	Output	PM_AF16	4A	B4A_NO	PM_AF16	2.5 V		12mA (default)	1 (default)
HEX2[6]	Output	PM_W16	4A	B4A_NO	PM_W16	2.5 V		12mA (default)	1 (default)
HEX2[5]	Output	PM_AF18	4A	B4A_NO	PM_AF18	2.5 V		12mA (default)	1 (default)
HEX2[4]	Output	PM_Y18	4A	B4A_NO	PM_Y18	2.5 V		12mA (default)	1 (default)
HEX2[3]	Output	PM_Y17	4A	B4A_NO	PM_Y17	2.5 V		12mA (default)	1 (default)
HEX2[2]	Output	PM_AA18	4A	B4A_NO	PM_AA18	2.5 V		12mA (default)	1 (default)
HEX2[1]	Output	PM_AB17	4A	B4A_NO	PM_AB17	2.5 V		12mA (default)	1 (default)
HEX2[0]	Output	PM_AA21	4A	B4A_NO	PM_AA21	2.5 V		12mA (default)	1 (default)
HEX3[6]	Output	PM_AD20	4A	B4A_NO	PM_AD20	2.5 V		12mA (default)	1 (default)
HEX3[5]	Output	PM_AA19	4A	B4A_NO	PM_AA19	2.5 V		12mA (default)	1 (default)
HEX3[4]	Output	PM_AC20	4A	B4A_NO	PM_AC20	2.5 V		12mA (default)	1 (default)
HEX3[3]	Output	PM_AA20	4A	B4A_NO	PM_AA20	2.5 V		12mA (default)	1 (default)
HEX3[2]	Output	PM_AD19	4A	B4A_NO	PM_AD19	2.5 V		12mA (default)	1 (default)
HEX3[1]	Output	PM_W19	4A	B4A_NO	PM_W19	2.5 V		12mA (default)	1 (default)
HEX3[0]	Output	PM_Y19	4A	B4A_NO	PM_Y19	2.5 V		12mA (default)	1 (default)
HEX4[6]	Output	PM_AH22	4A	B4A_NO	PM_AH22	2.5 V		12mA (default)	1 (default)
HEX4[5]	Output	PM_AF23	4A	B4A_NO	PM_AF23	2.5 V		12mA (default)	1 (default)
HEX4[4]	Output	PM_AG23	4A	B4A_NO	PM_AG23	2.5 V		12mA (default)	1 (default)
HEX4[3]	Output	PM_AE23	4A	B4A_NO	PM_AE23	2.5 V		12mA (default)	1 (default)
HEX4[2]	Output	PM_AE22	4A	B4A_NO	PM_AE22	2.5 V		12mA (default)	1 (default)

Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location	I/O Standard	Reserved	Current Strength	Slew Rate
HEX1[1]	Output	PM_V16	4A	B4A_NO	PM_V16	2.5 V		12mA (default)	1 (default)
HEX1[0]	Output	PM_AF16	4A	B4A_NO	PM_AF16	2.5 V		12mA (default)	1 (default)
HEX2[6]	Output	PM_W16	4A	B4A_NO	PM_W16	2.5 V		12mA (default)	1 (default)
HEX2[5]	Output	PM_AF18	4A	B4A_NO	PM_AF18	2.5 V		12mA (default)	1 (default)
HEX2[4]	Output	PM_Y18	4A	B4A_NO	PM_Y18	2.5 V		12mA (default)	1 (default)
HEX2[3]	Output	PM_Y17	4A	B4A_NO	PM_Y17	2.5 V		12mA (default)	1 (default)
HEX2[2]	Output	PM_AA18	4A	B4A_NO	PM_AA18	2.5 V		12mA (default)	1 (default)
HEX2[1]	Output	PM_AB17	4A	B4A_NO	PM_AB17	2.5 V		12mA (default)	1 (default)
HEX2[0]	Output	PM_AA21	4A	B4A_NO	PM_AA21	2.5 V		12mA (default)	1 (default)
HEX3[6]	Output	PM_AD20	4A	B4A_NO	PM_AD20	2.5 V		12mA (default)	1 (default)
HEX3[5]	Output	PM_AA19	4A	B4A_NO	PM_AA19	2.5 V		12mA (default)	1 (default)
HEX3[4]	Output	PM_AC20	4A	B4A_NO	PM_AC20	2.5 V		12mA (default)	1 (default)
HEX3[3]	Output	PM_AA20	4A	B4A_NO	PM_AA20	2.5 V		12mA (default)	1 (default)
HEX3[2]	Output	PM_AD19	4A	B4A_NO	PM_AD19	2.5 V		12mA (default)	1 (default)
HEX3[1]	Output	PM_W19	4A	B4A_NO	PM_W19	2.5 V		12mA (default)	1 (default)
HEX3[0]	Output	PM_Y19	4A	B4A_NO	PM_Y19	2.5 V		12mA (default)	1 (default)
HEX4[6]	Output	PM_AH22	4A	B4A_NO	PM_AH22	2.5 V		12mA (default)	1 (default)
HEX4[5]	Output	PM_AF23	4A	B4A_NO	PM_AF23	2.5 V		12mA (default)	1 (default)
HEX4[4]	Output	PM_AG23	4A	B4A_NO	PM_AG23	2.5 V		12mA (default)	1 (default)
HEX4[3]	Output	PM_AE23	4A	B4A_NO	PM_AE23	2.5 V		12mA (default)	1 (default)
HEX4[2]	Output	PM_AE22	4A	B4A_NO	PM_AE22	2.5 V		12mA (default)	1 (default)
HEX4[1]	Output	PM_AG22	4A	B4A_NO	PM_AG22	2.5 V		12mA (default)	1 (default)
HEX4[0]	Output	PM_AD21	4A	B4A_NO	PM_AD21	2.5 V		12mA (default)	1 (default)
HEX5[6]	Output	PM_AB21	4A	B4A_NO	PM_AB21	2.5 V		12mA (default)	1 (default)
HEX5[5]	Output	PM_AF19	4A	B4A_NO	PM_AF19	2.5 V		12mA (default)	1 (default)
HEX5[4]	Output	PM_AE19	4A	B4A_NO	PM_AE19	2.5 V		12mA (default)	1 (default)
HEX5[3]	Output	PM_AG20	4A	B4A_NO	PM_AG20	2.5 V		12mA (default)	1 (default)
HEX5[2]	Output	PM_AF20	4A	B4A_NO	PM_AF20	2.5 V		12mA (default)	1 (default)
HEX5[1]	Output	PM_AG21	4A	B4A_NO	PM_AG21	2.5 V		12mA (default)	1 (default)
HEX5[0]	Output	PM_AF21	4A	B4A_NO	PM_AF21	2.5 V		12mA (default)	1 (default)
clk	Input	PM_A14	3B	B3B_NO	PM_A14	2.5 V		12mA (default)	1 (default)

Hardware Implementation:

 

22B[EC1205]

Result:

The 7-segment display was successfully designed and implemented using Verilog on the DE10 FPGA board. The registration number 'EC1205' was displayed correctly on the 7-segment display using proper multiplexing and segment encoding techniques. The functionality was verified through simulation and hardware testing, ensuring correct digit transitions and adequate illumination of segments.